

## Lab 1: Digital Logic Gates

### Objectives

- To study the basic logic gates: AND, OR, INVERT, NAND, and NOR.
- To study the representation of these functions by truth tables, logic diagrams and Boolean algebra.
- To observe the pulse response of logic gates.
- To measure the propagation delay of logic gates.

### Apparatus

7400 Quadruple 2-input NAND gates  
 7402 Quadruple 2-input NOR gates  
 7404 Hex Inverters (x2)  
 7408 Quadruple 2-input AND gates  
 7432 Quadruple 2-input OR gates  
 7486 Quadruple 2-input XOR gate  
 CADET trainer  
 Dual-trace oscilloscope

### Theory

#### AND

A multi-input circuit in which the output is 1 only if all inputs are 1. The symbolic representation of the AND gate is shown in Fig. 1a.

#### OR

A multi-input circuit in which the output is 1 when any input is 1. The symbolic representation of the OR gate is shown in Fig. 1b.

#### INVERT

The output is 0 when the input is 1, and the output is 1 when the input is 0. The symbolic representation of an inverter is shown in Fig. 1c.

#### NAND

AND followed by INVERT. The symbolic representation of the NAND gate is shown in Fig 1d.

#### NOR

OR followed by INVERT as shown in Fig. 1e.

#### EX-OR

The output of the Exclusive –OR gate, is 0 when it's two inputs are the same and it's output is 1 when its two inputs are different, Fig. 1f.

### Truth Table

Representation of the output logic levels of a logic circuit for every possible combination of levels of the inputs. This is best done by means of a systematic tabulation.

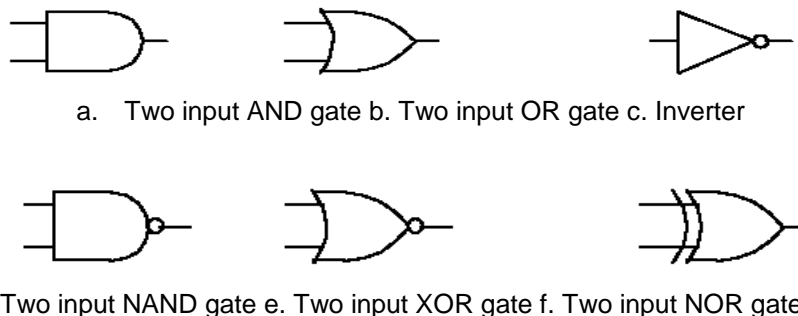


Fig. 1 Symbols for digital logic gates

**Part 1: Logic Functions****I. AND, OR, NAND, and NOR gates.**

1. Use one gate for each IC 7400 (NAND), 7402 (NOR), 7408 (AND), 7432 (OR), 7486 (XOR). Each has input pins\* 1 and 2, and output pin 3.
2. Connect pin 1 to switch S1-1, pin 2 to switch S1-2, and pin 3 to LED-1 for every gate as shown in Fig. 2 as an example for the NAND gate.

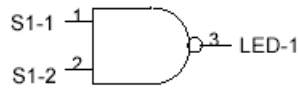


Fig. 2 Two input NAND gate

3. Using logic switches S1-1 and S-2, apply the logic levels 0 and 1 to gate inputs (pin 1, pin 2), in the sequence shown in Table 1. Record the output logic levels (see LED-1) in Table 1. Repeat the recordings for each gate. Remember: LED ON = Logic 1, (High) LED OFF = Logic 0 (Low)

Table 1

Pin 1	Pin 2	Pin 3

4. Use an inverter gate from IC 7404 whose input pin is pin 1 and whose output pin is pin 2.

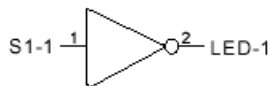


Fig. 3 Inverter gate

5. Using logic switches S1-1, apply the logic levels 0 and 1 in the sequence shown in Table 2. Record the output logic levels in Table 2.

Table 2

Pin 1	Pin 2
0	
1	
1	
0	

## Part-2: Response of Logic Gates:

Connect the circuits of Fig. 4 and 5 and write the corresponding truth tables 3 and 4, respectively.

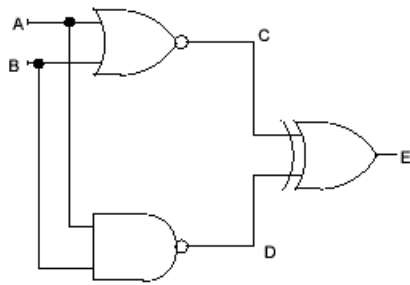


Fig. 4

Table 3

A	B	C	D	E
0	0			
0	1			
1	0			
1	1			

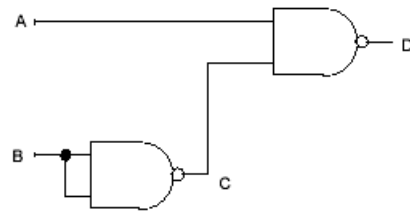






Fig. 5

Table 4

A	B	C	D
0	0		
0	1		
1	0		
1	1		

## Part 3: Review Questions:

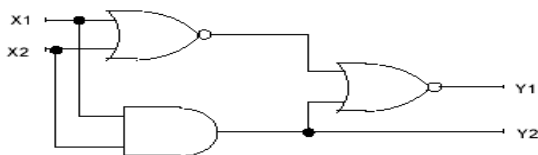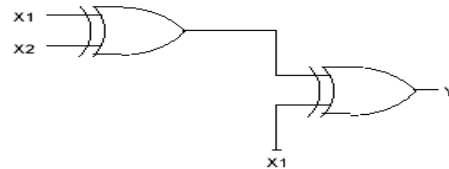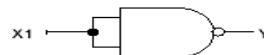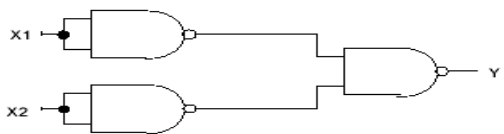1. Write a truth table for each circuit. Derive Boolean expressions for all outputs.



2. A burglar alarm for a car has a normally low switch on each of four doors. If any door is opened the output of that switch goes HIGH. The alarm is set off with an active-LOW output signal. What type of gate will provide this logic? Support your answer with an explanation.